

# EE-224: Digital Design

---

## Common Functions & Implementation

---

Virendra Singh

Professor

Computer Architecture and Dependable Systems Lab

Department of Electrical Engineering

Indian Institute of Technology Bombay

<http://www.ee.iitb.ac.in/~viren/>

E-mail: [viren@ee.iitb.ac.in](mailto:viren@ee.iitb.ac.in)



*Lecture 6: 31 August 2020*

**CADSL**

# Digital System

---



# Digital Logic Design

---

- Express input output relationship using **Truth table**
- Generate the logical expression by disjunction (OR) of terms (conjunction of variables – AND) where system evaluates to true
- Replace all operators by the logic gates
- Replace logic gates by equivalent switching network (e.g., transistor level circuit)



# Specification: Logic Expression

Truth Table

X Y Z	F
0 0 0	0
0 0 1	1
0 1 0	0
0 1 1	0
1 0 0	1
1 0 1	1
1 1 0	1
1 1 1	1

Logic Expression

$$F = \overline{X}.\overline{Y}.Z + X.\overline{Y}.\overline{Z} + X.\overline{Y}.Z \\ + X.\overline{Y}.Z + X.Y.Z$$





# Common Functions



# Enabling Function

- *Enabling* permits an input signal to pass through to an output
- *Disabling* blocks an input signal from passing through to an output, replacing it with a fixed value
- When disabled, 0 output
- When disabled, 1 output

EN	X	Y
0	0	0
0	1	0
1	0	0
1	1	1

  

# Decoding Function

---


- Decoding - the
  - Conversion of  $n$ -bit input to  $m$ -bit output
  - Given  $n \leq m \leq 2^n$
- Circuits that perform decoding are called *decoders*
  - Called  $n$ -to- $m$  line decoders, where  $m \leq 2^n$ , and
  - Generate  $2^n$  (or fewer) 1's in output for the  $n$  input variables



# Decoder

- 1-to-2-Line Decoder


A	D <sub>0</sub>	D <sub>1</sub>
0	1	0
1	0	1

 

- 2-to-4-Line Decoder

A <sub>1</sub>	A <sub>0</sub>	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

(a)

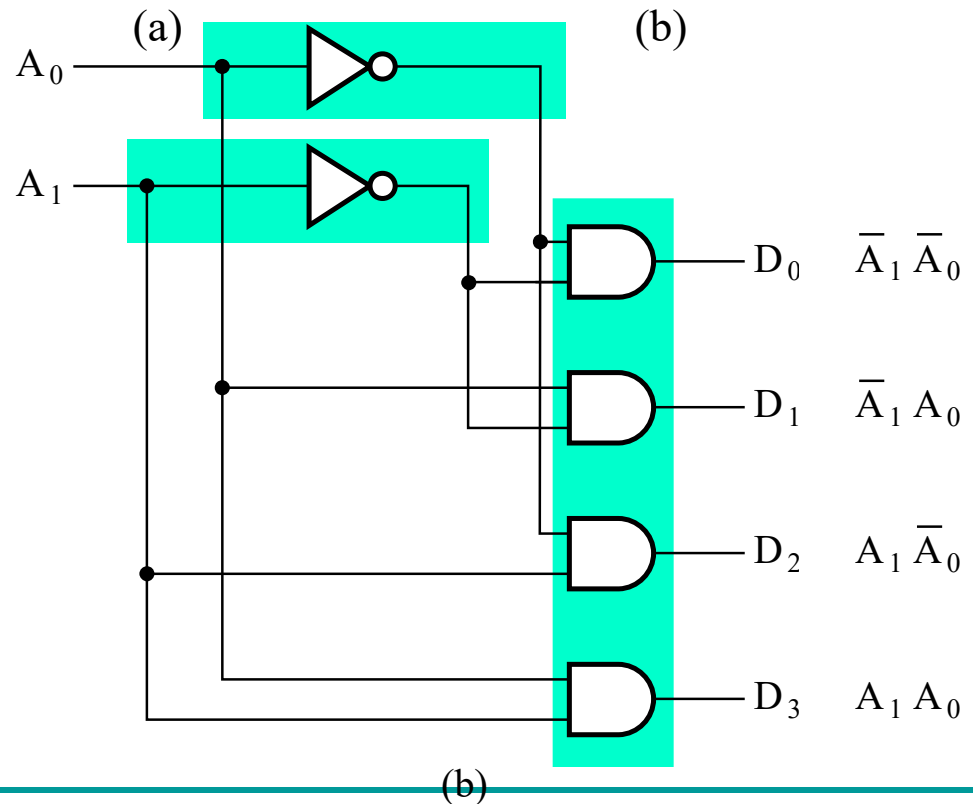

(b)



# Encoding Function

---

- Encoding - the opposite of decoding
  - Conversion of  $m$ -bit input to  $n$ -bit output
- Circuits that perform encoding are called *encoders*
  - An encoder has  $2^n$  (or fewer) input lines and  $n$  output lines which generate the binary code corresponding to the input values
  - Typically, an encoder converts a code containing exactly one bit that is 1 to a binary code corresponding to the position in which the 1 appears.



# Encoder

---

- A decimal-to-BCD encoder
  - Inputs: 10 bits corresponding to decimal digits 0 through 9, ( $D_0, \dots, D_9$ )
  - Outputs: 4 bits with BCD codes
  - Function: If input bit  $D_i$  is a 1, then the output ( $A_3, A_2, A_1, A_0$ ) is the BCD code for  $i$ ,
- The truth table could be formed, but alternatively, the equations for each of the four outputs can be obtained directly.



# Encoder

- Input  $D_i$  is a term in equation  $A_j$  if bit  $A_j$  is 1 in the binary value for  $i$ .

- Equations:

$$A_3 = D_8 + D_9$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_0 = D_1 + D_3 + D_5 + D_7 + D_9$$

0000
0001
0010
0011
0100
0101
0110
0111
1000
1001

# Selection Function


---

- Selecting of data or information is a critical function in digital systems and computers
- Circuits that perform selecting have:
  - A set of information inputs from which the selection is made
  - A single output
  - A set of control lines for making the selection
- Logic circuits that perform selecting are called **multiplexers**


 
# Multiplexers

- A **multiplexer** selects one input line and transfers it to output
  - $n$  control inputs ( $S_{n-1}, \dots S_0$ ) called *selection inputs*
  - $m \leq 2^n$  information inputs ( $I_{2^n-1}, \dots I_0$ )
  - output  $Y$



# 2-to-1-Line Multiplexer

- Since  $2 = 2^1$ ,  $n = 1$
- The single selection variable  $S$  has two values:

- $S = 0$  selects input  $I_0$
- $S = 1$  selects input  $I_1$

- Truth Table

- Symbolic equation:

$$Y = I_0 \cdot \bar{S} + S \cdot I_1$$

- Logic expression

$$Y = \bar{S} \cdot I_0 \cdot \bar{I}_1 + \bar{S} \cdot I_0 \cdot I_1 \\ + S \cdot \bar{I}_0 \cdot I_1 + S \cdot I_0 \cdot I_1$$

S	I <sub>0</sub>	I <sub>1</sub>	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1





# 2-to-1-Line Multiplexer

- The single selection variable  $S$  has two values:

- $S = 0$  selects input  $I_0$
- $S = 1$  selects input  $I_1$

- The logic equation:

$$Y = I_0 \bar{S} + S.I_1$$

  


# Implementation





# Using Logic Gates


- 2x1 Multiplexer

 

Truth Table

S	I <sub>0</sub>	I <sub>1</sub>	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

# Using Storage Elements

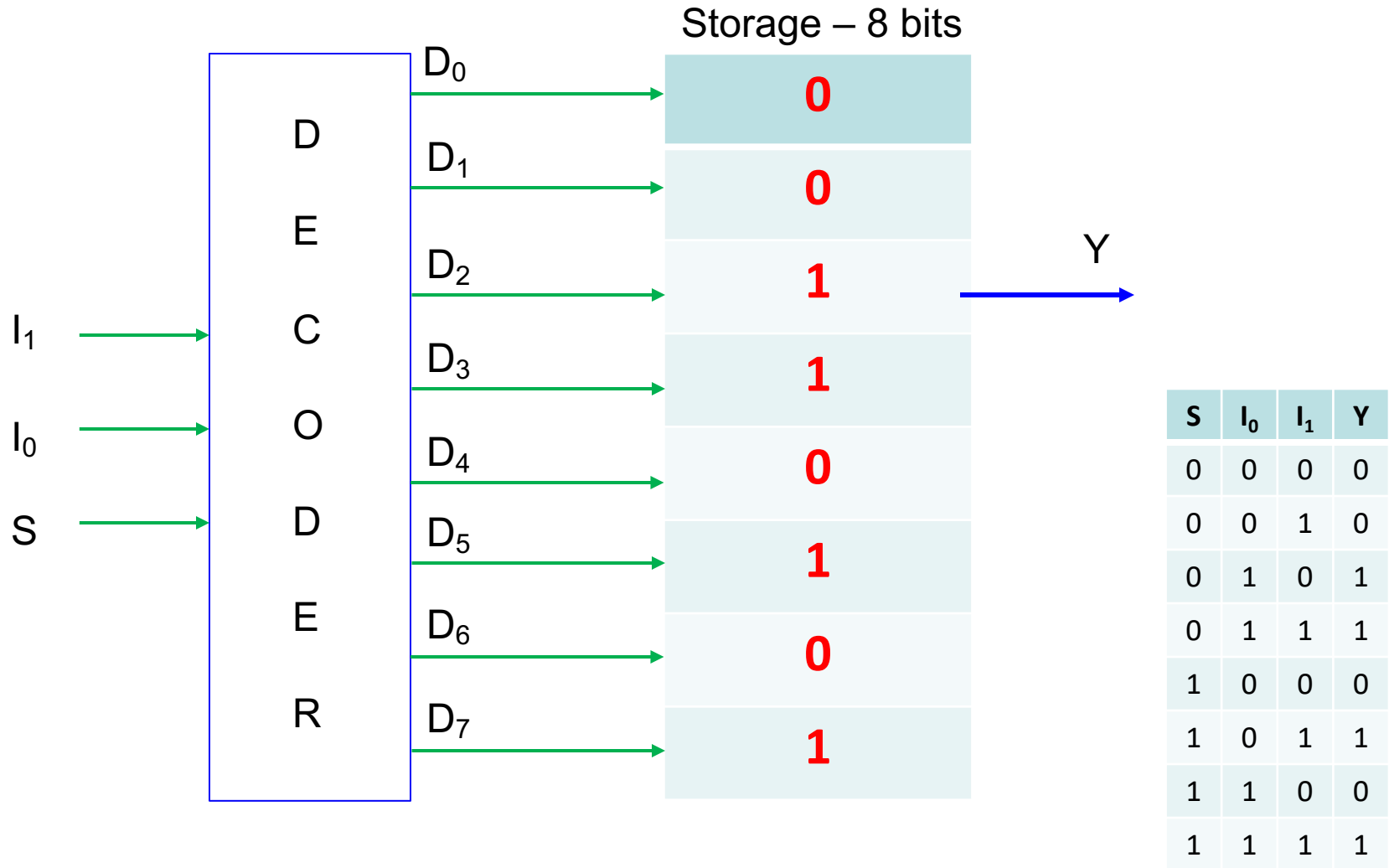

# Optimization



# Specification: Logic Function

Truth Table

X Y Z	F
0 0 0	0
0 0 1	1
0 1 0	0
0 1 1	0
1 0 0	1
1 0 1	1
1 1 0	1
1 1 1	1

Logic Expression


$$F = \overline{X}.\overline{Y}.Z + X.\overline{Y}.\overline{Z} + X.\overline{Y}.Z + \overline{X}.Y.Z + X.Y.Z$$



$$F = X + \overline{Y}.Z$$



Logic Diagram

 

# Optimization Parameters

---

- Area: # Switches (Gates)
- Performance (Delay): # Switches in series
- Power: # Switches
- Testability: Interconnect network
- Security
- Intelligence



# Thank You

