

Signal Processing - 1 by One

Sibi Raj B. Pillai
Dept of Electrical Engineering
IIT Bombay



- So Far: Sampling, Convolution, Fourier Transform
- Previous Week: Shannon Sampling Theorem
- Previous Class: Circuits, Systems and Laplace Transform
- Today: RLC Circuit, Parseval Revisited




- So Far: Sampling, Convolution, Fourier Transform
- Previous Week: Shannon Sampling Theorem
- Previous Class: Circuits, Systems and Laplace Transform
- Today: RLC Circuit, Parseval Revisited




Not-So Linear Initial Conditions

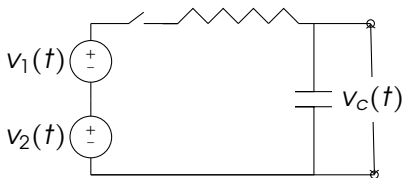Q4) Can you apply superposition theorem on the two voltage sources to find $v_c(t)$. The resistor is R ohms and capacitor is C Farads, which has an initial charge of 0.3V.



Not-So Linear Initial Conditions

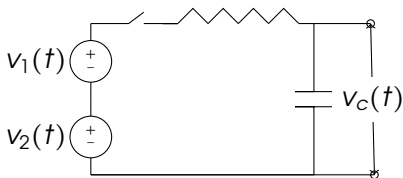Q4) Can you apply superposition theorem on the two voltage sources to find $v_c(t)$. The resistor is R ohms and capacitor is C Farads, which has an initial charge of 0.3V.



Solution: The important thing to notice that initial conditions can have an effect on the super-position principle, unless accounted properly. For example, consider the system $y(t) = ax(t) + c$, which appears *linear*, but should more aptly be called an *affine* system. Notice that

$$y_1(t) = ax_1(t) + c, y_2(t) = ax_2(t) + c \Rightarrow y_1(t) + y_2(t) = a(x_1(t) + x_2(t)) + 2c.$$


However, $x_1(t) + x_2(t)$ as input will produce $a(x_1(t) + x_2(t)) + c$ as output, which is different from $y_1(t) + y_2(t)$ (system *not linear*).

Similarly, in the circuit above, superposition should be applied after replacing the initial conditions by a suitable source signal.




RLC Circuit

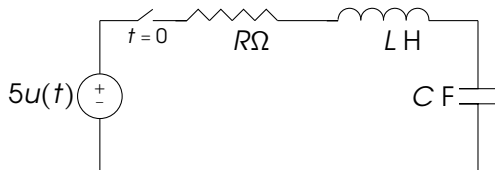Q5) For the serial RLC circuit find the voltage across C.



RLC Circuit

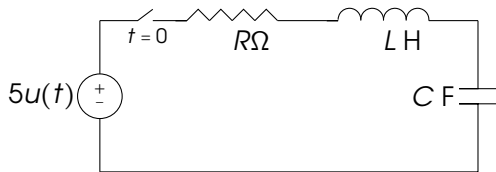Q5) For the serial RLC circuit find the voltage across C.




$$V_C(s) = \frac{V_i(s)}{R + sL + \frac{1}{sC}} \frac{1}{sC} = \frac{5}{LC} \frac{1}{s(s^2 + \frac{R}{L}s + \frac{1}{LC})}$$



RLC Circuit

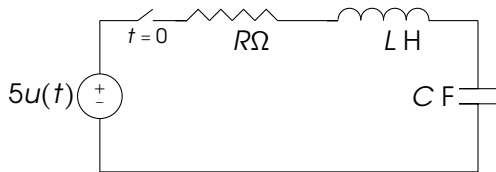Q5) For the serial RLC circuit find the voltage across C.




$$V_C(s) = \frac{V_i(s)}{R + sL + \frac{1}{sC}} \frac{1}{sC} = \frac{5}{LC} \frac{1}{s(s^2 + \frac{R}{L}s + \frac{1}{LC})} = 5 \left(\frac{1}{s} - \frac{s + \frac{R}{L}}{s + \frac{R}{L}s + \frac{1}{LC}} \right)$$



RLC Circuit

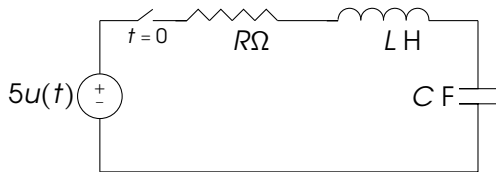Q5) For the serial RLC circuit find the voltage across C.




$$\begin{aligned} V_C(s) &= \frac{V_i(s)}{R + sL + \frac{1}{sC}} \frac{1}{sC} = \frac{5}{LC} \frac{1}{s(s^2 + \frac{R}{L}s + \frac{1}{LC})} = 5 \left(\frac{1}{s} - \frac{s + \frac{R}{L}}{s + \frac{R}{L}s + \frac{1}{LC}} \right) \\ &= 5 \left(\frac{1}{s} - \frac{s + \frac{R}{2L} + \frac{R}{2L}}{(s + \frac{R}{2L})^2 + \frac{1}{LC} - (\frac{R}{2L})^2} \right) \end{aligned}$$



RLC Circuit

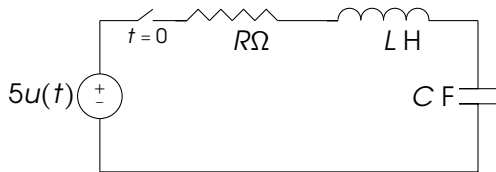Q5) For the serial RLC circuit find the voltage across C.




$$\omega^2 = \frac{1}{LC} - \left(\frac{R}{2L}\right)^2$$
$$\omega = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

$$V_C(s) = \frac{V_i(s)}{R + sL + \frac{1}{sC}} \frac{1}{sC} = \frac{5}{LC} \frac{1}{s(s^2 + \frac{R}{L}s + \frac{1}{LC})} = 5 \left(\frac{1}{s} - \frac{s + \frac{R}{L}}{s + \frac{R}{L}s + \frac{1}{LC}} \right)$$
$$= 5 \left(\frac{1}{s} - \frac{s + \frac{R}{2L} + \frac{R}{2L}}{(s + \frac{R}{2L})^2 + \frac{1}{LC} - (\frac{R}{2L})^2} \right)$$



RLC Circuit

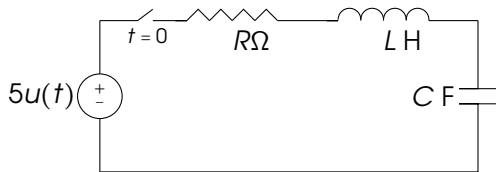Q5) For the serial RLC circuit find the voltage across C.



$$\omega^2 = \frac{1}{LC} - \left(\frac{R}{2L}\right)^2$$
$$\omega = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

$$V_C(s) = \frac{V_i(s)}{R + sL + \frac{1}{sC}} \frac{1}{sC} = \frac{5}{LC} \frac{1}{s(s^2 + \frac{R}{L}s + \frac{1}{LC})} = 5 \left(\frac{1}{s} - \frac{s + \frac{R}{L}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} \right)$$
$$= 5 \left(\frac{1}{s} - \frac{s + \frac{R}{2L} + \frac{R}{2L}}{(s + \frac{R}{2L})^2 + \frac{1}{LC} - (\frac{R}{2L})^2} \right)$$

$$v_C(t) = 5 \left[1 - \exp\left(-\frac{R}{2L}t\right) \cos(\omega t) - \frac{R}{2\omega L} \exp\left(-\frac{R}{2L}t\right) \sin(\omega t) \right] u(t), \omega > 0.$$



Parseval's Relation

$$\int_{\mathbb{R}} x(t) y^*(t) dt = \int_{\mathbb{R}} X(f) Y^*(f) df.$$

Proof:



Parseval's Relation

$$\int_{\mathbb{R}} x(t) y^*(t) dt = \int_{\mathbb{R}} X(f) Y^*(f) df.$$

Proof:

$$\int_{\mathbb{R}} x(t) y^*(t) dt = \int_{t \in \mathbb{R}} \int_{u \in \mathbb{R}} X(f) \exp(j2\pi ut) du \left(\int_{v \in \mathbb{R}} Y(v) \exp(j2\pi vt) dv \right)^* dt$$



Parseval's Relation

$$\int_{\mathbb{R}} x(t) y^*(t) dt = \int_{\mathbb{R}} X(f) Y^*(f) df.$$

Proof:

$$\begin{aligned} \int_{\mathbb{R}} x(t) y^*(t) dt &= \int_{t \in \mathbb{R}} \int_{u \in \mathbb{R}} X(f) \exp(j2\pi ut) du \left(\int_{v \in \mathbb{R}} Y(v) \exp(j2\pi vt) dv \right)^* dt \\ &= \int_{u \in \mathbb{R}} \int_{v \in \mathbb{R}} X(u) Y^*(v) \int_{t \in \mathbb{R}} \exp(j2\pi(u-v)t) dt dv du \end{aligned}$$



Parseval's Relation

$$\int_{\mathbb{R}} x(t) y^*(t) dt = \int_{\mathbb{R}} X(f) Y^*(f) df.$$

Proof:

$$\begin{aligned} \int_{\mathbb{R}} x(t) y^*(t) dt &= \int_{t \in \mathbb{R}} \int_{u \in \mathbb{R}} X(f) \exp(j2\pi ut) du \left(\int_{v \in \mathbb{R}} Y(v) \exp(j2\pi vt) dv \right)^* dt \\ &= \int_{u \in \mathbb{R}} \int_{v \in \mathbb{R}} X(u) Y^*(v) \int_{t \in \mathbb{R}} \exp(j2\pi(u-v)t) dt dv du \\ &= \int_{u \in \mathbb{R}} X(u) \int_{v \in \mathbb{R}} Y^*(v) \delta(u-v) dv du \end{aligned}$$



Parseval's Relation

$$\int_{\mathbb{R}} x(t) y^*(t) dt = \int_{\mathbb{R}} X(f) Y^*(f) df.$$

Proof:

$$\begin{aligned} \int_{\mathbb{R}} x(t) y^*(t) dt &= \int_{t \in \mathbb{R}} \int_{u \in \mathbb{R}} X(f) \exp(j2\pi ut) du \left(\int_{v \in \mathbb{R}} Y(v) \exp(j2\pi vt) dv \right)^* dt \\ &= \int_{u \in \mathbb{R}} \int_{v \in \mathbb{R}} X(u) Y^*(v) \int_{t \in \mathbb{R}} \exp(j2\pi(u-v)t) dt dv du \\ &= \int_{u \in \mathbb{R}} X(u) \int_{v \in \mathbb{R}} Y^*(v) \delta(u-v) dv du \\ &= \int_{u \in \mathbb{R}} X(u) Y^*(u) du. \end{aligned}$$



Parseval's Relation

$$\int_{\mathbb{R}} x(t) y^*(t) dt = \int_{\mathbb{R}} X(f) Y^*(f) df.$$

Proof:

$$\begin{aligned} \int_{\mathbb{R}} x(t) y^*(t) dt &= \int_{t \in \mathbb{R}} \int_{u \in \mathbb{R}} X(f) \exp(j2\pi ut) du \left(\int_{v \in \mathbb{R}} Y(v) \exp(j2\pi vt) dv \right)^* dt \\ &= \int_{u \in \mathbb{R}} \int_{v \in \mathbb{R}} X(u) Y^*(v) \int_{t \in \mathbb{R}} \exp(j2\pi(u-v)t) dt dv du \\ &= \int_{u \in \mathbb{R}} X(u) \int_{v \in \mathbb{R}} Y^*(v) \delta(u-v) dv du \\ &= \int_{u \in \mathbb{R}} X(u) Y^*(u) du. \end{aligned}$$

$$\int_{\mathbb{R}} |x(t)|^2 dt = \int_{\mathbb{R}} |X(f)|^2 df.$$



Worked Example

Question) Find the integral

$$\int_{t \in \mathbb{R}} \text{sinc}(2\alpha t) \text{sinc}^2(\alpha t) dt$$

