

Signal Processing - 1 by One

Sibi Raj B. Pillai
Dept of Electrical Engineering
IIT Bombay



- So Far: Sampling and Convolution
- Previous Week: Fourier Series and Fourier Transform
- Previous Class: Shannon Sampling Theorem
- Today: Frequency Concepts, Laplace Transform



- So Far: Sampling and Convolution
- Previous Week: Fourier Series and Fourier Transform
- Previous Class: Shannon Sampling Theorem
- Today: Frequency Concepts, Laplace Transform



Sampling Revisited

If $X(f)$ and $X(f + k\beta)$ does not overlap for any $k \in \mathbb{Z} \setminus \{0\}$,

$$X(f) = \text{rect}_\beta(f - f_0) \times \sum_{n \in \mathbb{Z}} X(f + n\beta).$$



Sampling Revisited

If $X(f)$ and $X(f + k\beta)$ does not overlap for any $k \in \mathbb{Z} \setminus \{0\}$,

$$X(f) = \text{rect}_\beta(f - f_0) \times \sum_{n \in \mathbb{Z}} X(f + n\beta).$$

If $f_0 = 0$:

$$x(t) = I.F.T[\text{rect}_\beta(f)] * I.F.T\left[\sum_{n \in \mathbb{Z}} X(f + n\beta)\right]$$



Sampling Revisited

If $X(f)$ and $X(f + k\beta)$ does not overlap for any $k \in \mathbb{Z} \setminus \{0\}$,

$$X(f) = \text{rect}_\beta(f - f_0) \times \sum_{n \in \mathbb{Z}} X(f + n\beta).$$

If $f_0 = 0$:

$$\begin{aligned} x(t) &= I.F.T \left[\text{rect}_\beta(f) \right] * I.F.T \left[\sum_{n \in \mathbb{Z}} X(f + n\beta) \right] \\ &= \beta \text{sinc}(\beta t) * \sum_{m \in \mathbb{Z}} \frac{1}{\beta} x\left(\frac{m}{\beta}\right) \delta\left(t - \frac{m}{\beta}\right) \end{aligned}$$



Sampling Revisited

If $X(f)$ and $X(f + k\beta)$ does not overlap for any $k \in \mathbb{Z} \setminus \{0\}$,

$$X(f) = \text{rect}_\beta(f - f_0) \times \sum_{n \in \mathbb{Z}} X(f + n\beta).$$

If $f_0 = 0$:

$$\begin{aligned} x(t) &= I.F.T[\text{rect}_\beta(f)] * I.F.T\left[\sum_{n \in \mathbb{Z}} X(f + n\beta)\right] \\ &= \beta \text{sinc}(\beta t) * \sum_{m \in \mathbb{Z}} \frac{1}{\beta} x\left(\frac{m}{\beta}\right) \delta\left(t - \frac{m}{\beta}\right) \\ &= \sum_{m \in \mathbb{Z}} x\left(\frac{m}{\beta}\right) \text{sinc}(\beta t - m). \end{aligned}$$



What is Frequency

Positive frequency: f Hz \Rightarrow f sinusoidal cycles per second .

Question: How about $\cos(2\pi ft + \theta)$ (Is this also $+f$ Hz?)



What is Frequency

Positive frequency: f Hz \Rightarrow f sinusoidal cycles per second .

Question: How about $\cos(2\pi ft + \theta)$ (Is this also $+f$ Hz?)



What is Frequency

Positive frequency: f Hz \Rightarrow f sinusoidal cycles per second .

Question: How about $\cos(2\pi ft + \theta)$ (Is this also $+f$ Hz?)

$$\cos(2\pi ft + \theta) = \cos(2\pi ft) \cos(\theta) - \sin(2\pi ft) \sin(\theta).$$



What is Frequency

Positive frequency: f Hz \Rightarrow f sinusoidal cycles per second .

Question: How about $\cos(2\pi ft + \theta)$ (Is this also $+f$ Hz?)

$$\cos(2\pi ft + \theta) = \cos(2\pi ft) \cos(\theta) - \sin(2\pi ft) \sin(\theta).$$

Notice that

$$\int_{k\frac{T}{2}}^{(k+1)\frac{T}{2}} \cos(2\pi ft) \sin(2\pi ft) dt = 0 \text{ for } T = \frac{1}{f}, k \in \mathbb{Z}.$$

Furthermore

$$\lim_{T_s \rightarrow \infty} \int_{-T_s}^{T_s} \cos(2\pi ft) \sin(2\pi ft) dt = 0 \text{ (In a generalized sense)}$$

$$\lim_{T_s \rightarrow \infty} \int_{-T_s}^{T_s} \cos(2\pi f_1 t) \sin(2\pi f_2 t) dt = 0 \text{ (as a generalized integral) .}$$



Frequency Components

A *real sinusoid* of frequency f has 2 orthogonal components:

$$\{\cos 2\pi ft, \sin 2\pi ft\}.$$



Frequency Components

A *real sinusoid* of frequency f has 2 orthogonal components:

$$\{\cos 2\pi f t, \sin 2\pi f t\}.$$

For a real $x(t)$, the 2 frequency components at f is represented by

$$a + jb = \int_{\mathbb{R}} x(t) (\cos 2\pi f t - j \sin 2\pi f t) dt = X(f).$$



Frequency Components

A *real sinusoid* of frequency f has 2 orthogonal components:

$$\{\cos 2\pi f t, \sin 2\pi f t\}.$$

For a real $x(t)$, the 2 frequency components at f is represented by

$$a + jb = \int_{\mathbb{R}} x(t) (\cos 2\pi f t - j \sin 2\pi f t) dt = X(f).$$

Notice that since

$$\cos(2\pi f t) = \frac{1}{2} (\exp(j2\pi f t) + \exp(-j2\pi f t)),$$

we need a $-f$ Hz component as well to represent $\cos(2\pi f t)$.



Frequency Components

A real sinusoid of frequency f has 2 orthogonal components:

$$\{\cos 2\pi f t, \sin 2\pi f t\}.$$

For a real $x(t)$, the 2 frequency components at f is represented by

$$a + jb = \int_{\mathbb{R}} x(t) (\cos 2\pi f t - j \sin 2\pi f t) dt = X(f).$$

Notice that since

$$\cos(2\pi f t) = \frac{1}{2} (\exp(j2\pi f t) + \exp(-j2\pi f t)),$$

we need a $-f$ Hz component as well to represent $\cos(2\pi f t)$.


For $f > 0$, if the component $\exp(-j2\pi f t)$ corresponds to positive frequency, then $\exp(j2\pi f t)$ corresponds to negative frequency

Notice that $\exp(-j2\pi f t)$ and $\exp(j2\pi f t)$ are orthogonal for $f > 0$.



Complex Circuits

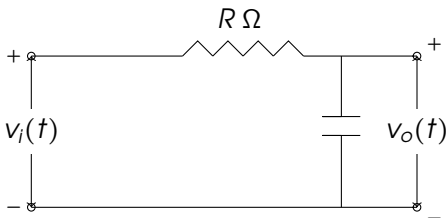Complex numbers in electrical circuits suggest the presence of both $\cos(2\pi ft)$ and $\sin(2\pi ft)$ inside, even when $\cos(2\pi ft)$ is input.



Generalizing the Fourier Transform: For $s = \sigma + j2\pi f$,

$$X(s) = \int_{\mathbb{R}} x(t) \exp(-st) dt \text{ (Two-sided Laplace Transform).}$$

Region of Convergence (ROC) : $\{ \text{Real}(\sigma) \}$ s.t. Integral exists.

$$\lim_{\sigma \rightarrow 0} X(s) = X(f).$$



Circuits and Systems

Kirchoff's Voltage Law:

$$v_i(t) = i(t) R + \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau.$$



Circuits and Systems

Kirchoff's Voltage Law:

$$v_i(t) = i(t) R + \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau.$$

Taking Laplace Transform (Two-sided)

$$V_i(s) = I(s) R + \frac{1}{C} \frac{I(s)}{s} \quad \text{and} \quad V_o(s) = \frac{1}{C} \frac{I(s)}{s}.$$



Circuits and Systems

Kirchoff's Voltage Law:

$$v_i(t) = i(t)R + \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau.$$

Taking Laplace Transform (Two-sided)

$$V_i(s) = I(s)R + \frac{1}{C} \frac{I(s)}{s} \quad \text{and} \quad V_o(s) = \frac{1}{C} \frac{I(s)}{s}.$$

$$V_o(s) = V_i(s) \frac{1}{1 + sRC}.$$



Circuits and Systems

Kirchoff's Voltage Law:

$$v_i(t) = i(t)R + \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau.$$

Taking Laplace Transform (Two-sided)

$$V_i(s) = I(s)R + \frac{1}{C} \frac{I(s)}{s} \quad \text{and} \quad V_o(s) = \frac{1}{C} \frac{I(s)}{s}.$$

$$V_o(s) = V_i(s) \frac{1}{1 + sRC}.$$


At $s = j2\pi f$,

$$V_o(f) = H(f) V_i(f) \quad \text{where} \quad H(f) = \frac{1}{1 + j2\pi fRC}$$

$$v_o(t) = h(t) * v_i(t) \quad \text{where} \quad h(t) = \frac{1}{RC} \exp\left(-\frac{t}{RC}\right), t \geq 0.$$



Laplace with Initial Conditions

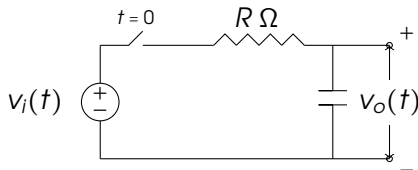

$$X(s) = \int_0^{\infty} x(t) \exp(-jst) dt$$

$$v_i(t) = i(t)R + \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau.$$

$$v_i'(t) = i'(t)R + \frac{1}{C} i(t)$$

$$sV_i(s) - v_i(0) = sRI(s) - i(0) + \frac{1}{C} I(s)$$

